

Total No. of Pages: 03

Roll No. ....

18

FIRST SEMESTER

B.Tech. (Group-A)

END SEMESTER EXAMINATION

(November-2014)

EE-105 ELECTRICAL SCIENCES

Time: 3:00 Hours

Max. Marks: 70

Note: Answer any Five questions. All questions carry equal marks.  
Assume the missing data suitably (if any)

- 1(a) Derive a relation for obtaining the delta connected formation of three resistances equivalent to star connected formation of three resistances. [6]
- (b) A current of 20 A flows through two ammeters A and B joined in series. The potential difference between A and B is 0.2 V and 0.3 V respectively. Find how the same current will divide between A and B when they are joined in parallel. [8]
- 2(a) State and illustrate with the help of an example the Tellegen's Theorem for electrical networks. [6]
- (b) Determine the loop current of the network as shown in Fig. 1. [8]

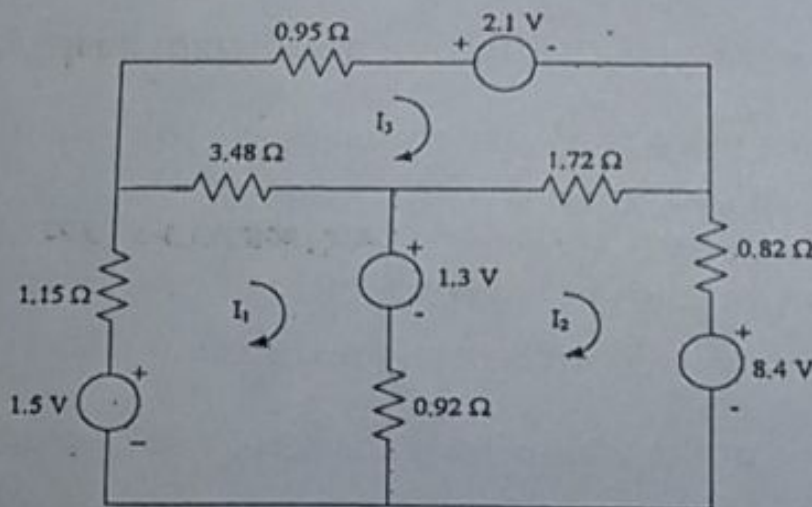


Fig. 1

- 3(a) Enumerate the advantages of using sinusoidal waveform for electric power supply. [6]
- (b) In the circuit shown in Fig. 2. What value of voltage ( $V_\theta$ ) applied across A-B will cause a current of  $10 \angle 0^\circ$  A to flow in the capacitor. Assume that the frequency of voltage applied as 50 Hz. [8]

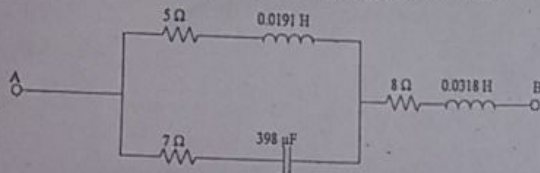


Fig. 2

- 4(a) Define series resonance in AC circuits. Draw the graphs showing variation of resistance, inductive reactance, capacitive reactance, total impedance and current with frequency. [6]
- (b) A coil of resistance  $40 \Omega$  and inductance of  $0.75$  H forms part of a series circuit for which resonant frequency is  $55$  Hz. If the supply voltage is  $250$  V,  $50$  Hz, find the line current, power factor and voltage across the coil. [8]
- 5 (a) Answer the following questions in reference to measurement of power using two single-phase wattmeter in  $3 \phi$  circuits. [6]
- (i) How will you measure reactive power in three phase circuits?
- (ii) What would be the readings of two wattmeter in this experiment if load is purely resistive?
- (iii) What would be the readings of two wattmeter in this experiment if load is purely reactive?
- (iv) If one of the wattmeter reads zero, what would be the power factor of the load?

- (b) A balanced  $3 \phi$  star connected load of  $150$  kW takes a leading current of  $100$  A with line voltage of  $1100$  V,  $50$  Hz. Find the constants of load. [8]
- 6(a) What are the different losses in a transformer? Explain how these losses can be minimized? [6]
- (b) A  $2500/250$  V,  $25$  kVA transformer has a core loss of  $130$  W and full load copper loss of  $320$  W. Calculate the maximum efficiency this transformer can exhibit. Also, determine the load kVA under this condition; consider the power factor of the load as unity. [8]
- 7 Explain the construction and principle of working of any two of the following: [2x7]
- (a) Permanent magnet moving coil ammeter
- (b) Multimeter
- (c) Digital Voltmeter
- (d) AC Watt-hour meter
8. Write notes on any two of the following [2x7]
- (a) Extension of range of voltmeter and ammeter
- (b) Dependent sources
- (c) Thevenin's Theorem
- (d) Analogy between electric and magnetic circuits

xxxxxxxxxxxxx