



EE 102
ELECTRICAL

Aditya Singh


2K19/A14/35

Assignment No-2

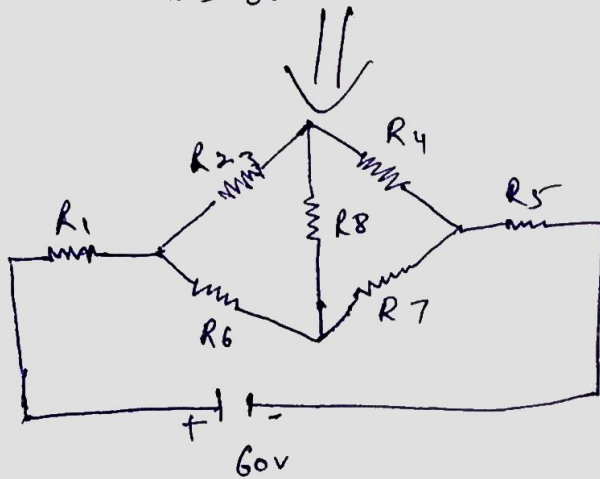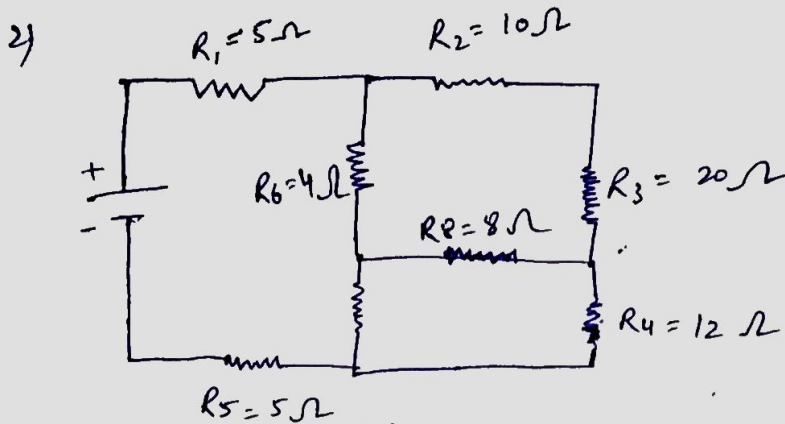Ans 1 To find = current delivered by battery.



Using Δ -Y Configuration transformation.



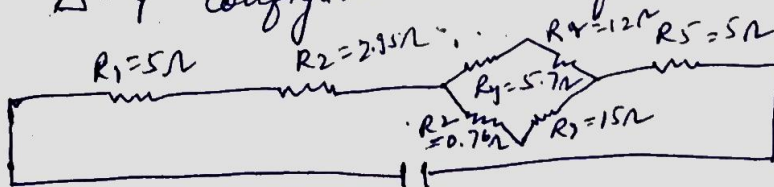


$$\text{Now, Current} = \frac{60}{R_{eq}} ; R_{eq} = R_1 + R_x + R_5 + \left(\frac{1}{R_4 + R_2} + \frac{1}{R_7 + R_6} \right)$$


$$\text{Current} = 3.324 \text{ A.}$$

Ans 2 To find thevenin equivalent circuit

Converting 10V and 20Ω to
Current source.

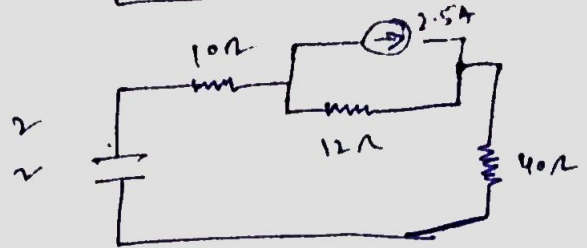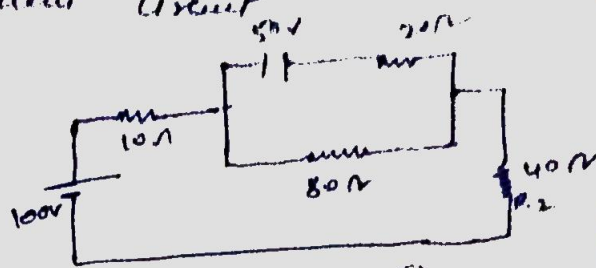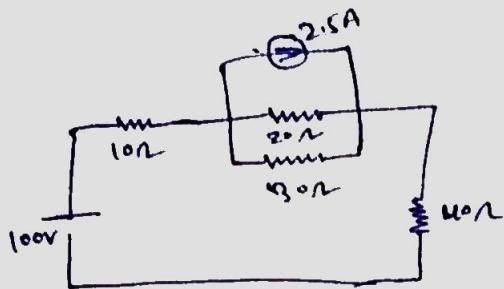


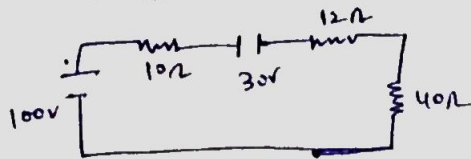Converting 2.5A Current source to Voltage source.



Now adding the Voltage source, we
have the required thevenin circuit
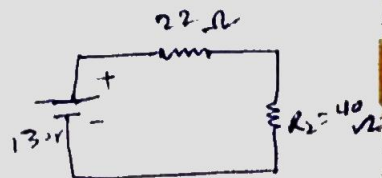
$$R_1 = 40\Omega \quad R_{th} = 22\Omega$$



Ans 3 To find: Current through 30Ω resistor

Assuming Current i_1, i_2 & i_3 .

for ABGHA \rightarrow

$$7 = 40i_1 + 30i_2 + 90i_3$$

for BCFG B \rightarrow

$$270i_1 = 90i_1 + 180i_3$$


for CDEFC \rightarrow

$$36 = 216i_3 - 180i_2$$

Solving 3 eqns

$$i_1 = \frac{37}{25} \text{ A}; \quad i_2 = \frac{34}{25} \text{ A}; \quad i_3 = \frac{13}{10} \text{ A} \therefore \text{Through } 90\Omega \text{ resistor}$$

$$i_{out} = \frac{3}{25} \text{ A}$$

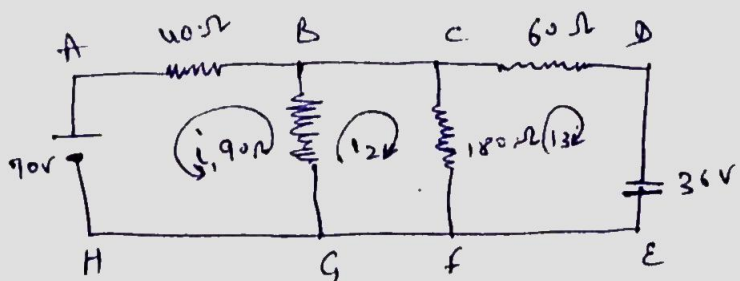


Ans 4 To solve for current using superposition shorting \mathcal{E}_2 and \mathcal{E}_3 .

$$i_1 = \frac{10}{17.42} = 0.579 \text{ A} \rightarrow 3\Omega$$

$$0.825 \rightarrow 6\Omega, 0.245 \rightarrow 8\Omega$$

$$0 \text{ A} \rightarrow 12\Omega$$

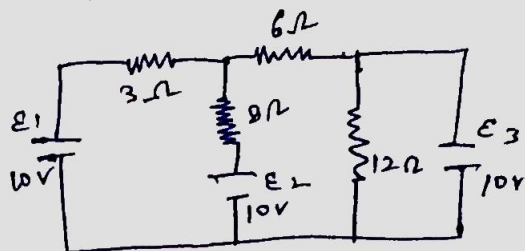

shorting \mathcal{E}_1 and \mathcal{E}_3 .


$$i_3 = 1.42 \text{ A} \rightarrow \text{total}$$

$$12\Omega \rightarrow 0.84 \text{ A}, 6\Omega \rightarrow 0.58 \text{ A}, 3\Omega \rightarrow -0.42 \text{ A}, 8\Omega \rightarrow 0.16 \text{ A}$$


Adding all we have

$12\Omega \rightarrow 0.84 \text{ A}$	top to bottom
$8\Omega \rightarrow 0.591 \text{ A}$	top to bottom
$6\Omega \rightarrow 0.79 \text{ A}$	left to right
$3\Omega \rightarrow 0.573 \text{ A}$	left to right

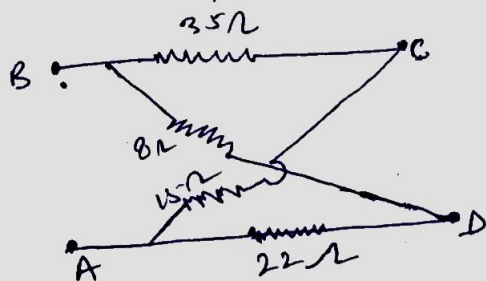Ans 5 To find equivalent resistance b/w A and B



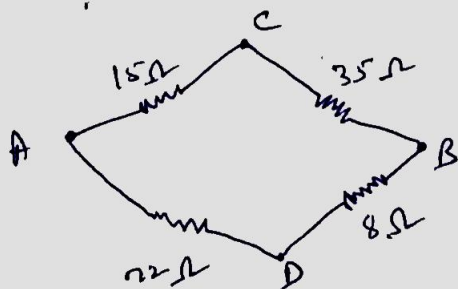
\Rightarrow The circuit can be resolved as.



solving

$$R_{eq} = \frac{50 \times 30}{50 + 30} = 18.75 \Omega$$

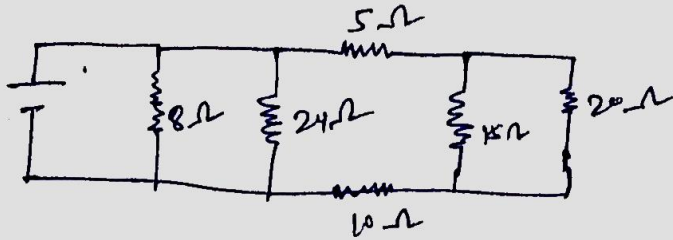Ans 6 To find: \mathcal{E} for power Consumption 180W in 20Ω



for making Thevenin equivalent circuit, short circuit 20Ω and finding eq resistance.



New potential drop across $20\Omega = \mathcal{E}$

Power $= i_2 R$, $i = \frac{\mathcal{E}}{4} A$, through: $20 = \left(\frac{\mathcal{E}}{4}\right)$

$$= 180 = \frac{\mathcal{E}^2}{20+20} \times 20 \rightarrow \boxed{\mathcal{E} = 60V}$$

Ans 7 find current through $R_2 = 20\Omega$

Shorting \mathcal{E}_2 ; we have

$i_1 = 2A \rightarrow \text{total}$


$=$ through $R_2 = 1A$, top to bottom

Shorting \mathcal{E}_1 .


$i_2 = 3A \rightarrow \text{total}$

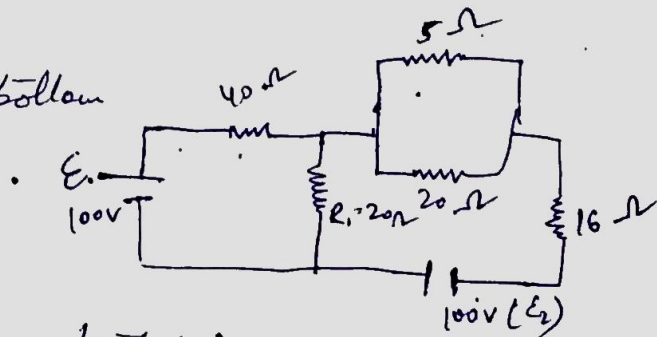2) through $R_2 = 2A$ (bottom to top)

Net current through $R_2 = 1A$. bottom to top.



8)

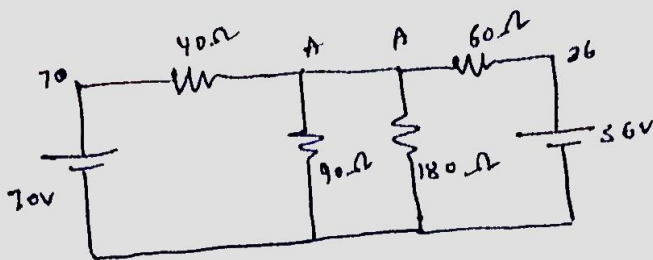

At Node A,


$$\frac{V_A - 70}{40} + \frac{V_A}{90} + \frac{V_A}{180} + \frac{V_A - 36}{60} = 0$$

$$V_A = 40.285 \text{ V}$$

Current through 90Ω ,

$$\frac{V_A}{90} = 0.448 \text{ A}$$

9)

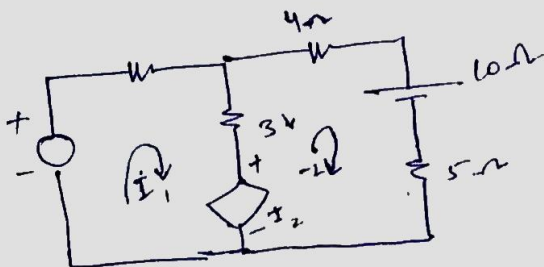

Using mesh analysis

$$\begin{bmatrix} 2+3-3 \\ -3, 3+4+5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10\text{V} \\ V-10 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 5 & -3 \\ -3 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10-V \\ V-10 \end{bmatrix}$$

Constraint of V

$$V = 2I_2 \Rightarrow I_2 (\alpha=1)$$

$$5I_1 - 3I_2 = 10 - I_2 \Rightarrow 5I_1 - 2I_2 = 10 \quad \text{--- (1)}$$


$$-3I_1 + 12I_2 = I_2 - 10 \Rightarrow +3I_1 - 11I_2 = +10 \quad \text{--- (2)}$$

$$\textcircled{1} \times 11 - \textcircled{2} \times 2$$


$$\Rightarrow 55I_1 - 6I_2 = 90$$

$$49I_1 = 90$$
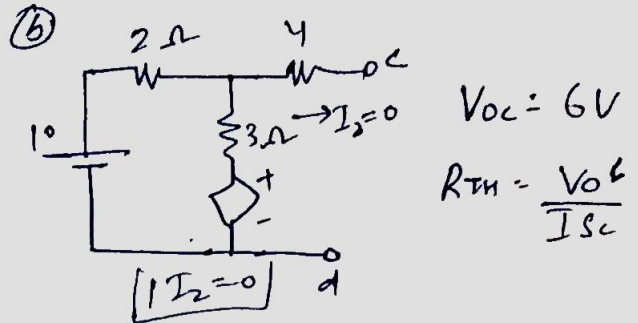
$$\textcircled{9} \quad I_1 = \frac{90}{49} = 1.83 \text{ A}$$



for I_{sc}

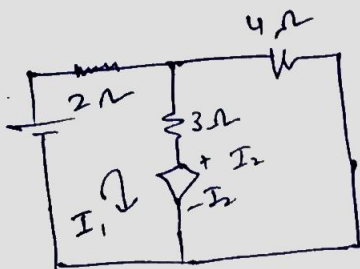

$$10 - 2I_1 - 3(I_1 - I_2) - I_2 = 0$$

$$\Rightarrow 5I_1 - 2I_2 = 10 \quad \text{--- (1)}$$

$$I_2 + 3(I_1 - I_2) - 4I_2 = 0$$

$$3I_1 - 6I_2 = 0$$


$$\boxed{I_1 = 2I_2}$$

$$10I_2 - 2I_2 = 10$$

$$I_2 = \frac{5}{4} \text{ A}$$


$$R_{TH} \Rightarrow \frac{6 \times 4}{5} = \frac{24}{5} \Omega \quad \underline{\text{Ans}}$$

Hence, thevenin eq.
Circuit

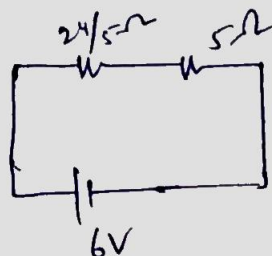

Ans

10

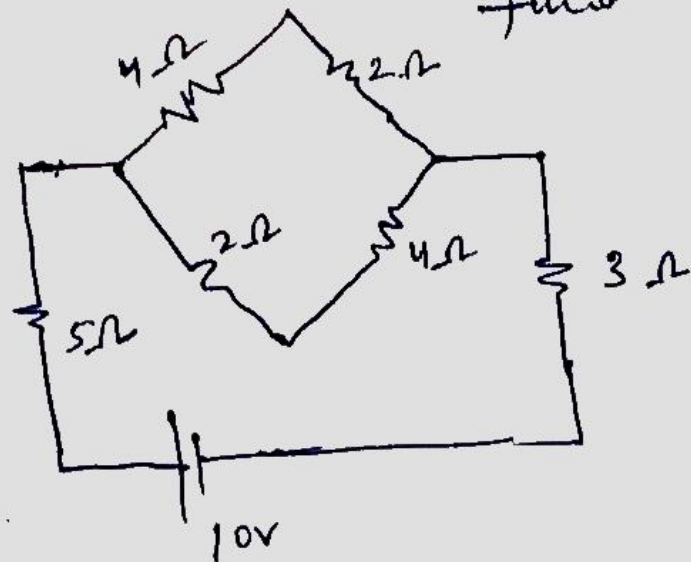

find the Current through 3Ω resistor

It satisfy condition for balanced wheat stone bridge
hence $I = 0$.

$$R_{eq} = 5 + \frac{6 \times 6}{6 + 6} + 3$$

$$R_{eq} \Rightarrow 11 \Omega$$

$$I_1 = \frac{10}{11} = 0.909.$$

$$I \text{ through } 3 \Omega \text{ resistor} = 0.91 \text{ Ans}$$