



Basic Electrical Engg – EE102

(Lecture Notes – Single Ph. AC Ckt)

Numerical Examples

- Phasor Representation of Sinusoidals
- Examples of Single Phase Series and Parallel Circuits

Dr Mini Sreejeth, Lecture Notes – Single Phase AC Circuits

1

1



Phasor Representation of Sinusoidals

- 1) Two sinusoidal currents are described as $i_1 = 10\sqrt{2} \sin \omega t$ and $i_2 = 20\sqrt{2} \sin(\omega t + 60^\circ)$. Find the expression for the sum of these currents.

$$i_1 = 10\sqrt{2} \sin \omega t = I_{m1} \sin \omega t \dots \dots \dots (1)$$

$$\text{Where } I_{m1} = 10\sqrt{2} \Rightarrow I_{1rms} = 10$$

$$i_2 = 20\sqrt{2} \sin(\omega t + 60^\circ) = I_{m2} \sin \omega t \dots \dots \dots (2)$$

$$\text{Where } I_{m2} = 20\sqrt{2}(\cos 60^\circ + j \sin 60^\circ)$$

$$= 20\sqrt{2} \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = 10\sqrt{2} + j10\sqrt{6}$$

$$\therefore I_m = I_{m1} + I_{m2} = 10\sqrt{2} + 10\sqrt{2} + j10\sqrt{6} = 20\sqrt{2} + j10\sqrt{6}$$

$$I_m = I_m \angle \theta ; I_m = \sqrt{(20\sqrt{2})^2 + (10\sqrt{6})^2} = 37.4 \quad \& \quad \tan^{-1} \frac{10\sqrt{6}}{20\sqrt{2}} = 41^\circ$$

$$I_m = 37.4 \angle 41^\circ$$

$$\therefore i = 37.4 \sin(\omega t + 41^\circ)$$

Dr Mini Sreejeth, Lecture Notes – Single Phase AC Circuits

2

2



Phasor Representation of Sinusoids

- 2) A sinusoidal current having an effective value of $10\angle 0^\circ A$ is added to another sinusoidal current of effective value $20\angle 60^\circ A$. Find the effective value of the resultant current.

$$\begin{aligned} I &= I_1 + I_2 = 10\angle 0^\circ + 20\angle 60^\circ = 10 + 20 (\cos 60^\circ + j\sin 60^\circ) \\ &= 20 + j10\sqrt{3} = 26.4\angle 41^\circ \end{aligned}$$

$$\therefore i = \sqrt{2} (26.4) \sin (\omega t + 41^\circ) = 37.4 \sin (\omega t + 41^\circ)$$



Other Examples of Single Phase Series and Parallel Circuits



Example 1

A voltage $(80 + j60)V$ is applied to a series circuit and the current is $(-4 + j10)A$.

- (a) Find Z , power factor and active power.
- (b) Is the circuit inductive or capacitive ?
- (c) Find the parameters of the circuit if $f=50\text{Hz}$.



Example 1

Solution

$$V = 80 + j60 = 100 \angle 36.87^\circ V$$

$$I = -4 + j10 = 10.77 \angle 111.8^\circ$$

a) $Z = \frac{V}{I} = \frac{100 \angle 36.87^\circ}{10.77 \angle 111.8^\circ} = 9.825 \angle -74.93^\circ \Omega$
 $pf = \cos \theta = \cos (-74.93) = 0.26 \text{ leading}$
 $P = VI \cos \theta = 100 \times 10.77 \times 0.26 = 280 W$

b) Current phasor is leading the voltage phasor. The current is capacitive

c) $R = Z \cos \theta = 9.825 \times 0.26 = 2.55 \Omega$

$$C = \frac{1}{\omega X_c} = \frac{1}{2\pi \times 50 \times 9.49} = 335.4 \times 10^{-4} F$$



Example 2

A parallel RL circuit has a $6\ \Omega$ resistance in one branch and a $0.05\ H$ inductance in the other. It is excited by a $230\ V$, $50\ Hz$ ac supply. Find

- a) The circuit current.
- b) Z
- c) Y
- d) Power factor, apparent, active and reactive power and
- e) Parameters of the equivalent series circuit



Example 2

Solution

$$a) \quad I_r = \frac{230\angle 0^\circ}{6} = 38.33\angle 0^\circ\ A$$

$$I_L = \frac{V}{jX_L} = \frac{230\angle 0^\circ}{j(2\pi \times 50 \times 0.05)} = 14.64\angle -90^\circ\ A$$

$$I = I_r + I_L = 38.33 - j14.66\ A = 41.03\angle -20.9^\circ\ A$$

$$b) \quad Z = \frac{V}{I} = \frac{230}{41.03\angle -20.9^\circ} = 5.61\angle 20.9^\circ\ \Omega$$

$$c) \quad Y = \frac{1}{Z} = \frac{1}{5.61\angle 20.9^\circ} = 0.178\angle -20.9^\circ\ \text{siemen}$$



Example 2

Solution (contd...)

d) $pf = \cos(-20.9^\circ) = 0.934 \text{ lagging}$

$\text{Apparent power} = VI = 230 \times 41.03 = 9436.9 \text{ VA}$

$\text{Active power} = VI \cos\theta = 9436.9 \times 0.934 = 8814.06 \text{ W}$

$\text{Reactive power} = VI \sin\theta = 9436.9 \times \sin 20.9^\circ = 3366.5 \text{ vars (inductive)}$

e) $Z = 5.61 \angle 20.9^\circ = 5.24 + j2 \Omega$

$R_{eq} = 5.24 \Omega$


$X_{eq} = 2 \Omega$

$L_{eq} = \frac{2}{2\pi \times 50} = 0.00637 \text{ H}$



Example 3

Determine the load current in the circuit given in Fig. Also, determine the source voltage and load current delivered by the source. Calculate power, reactive power and volt-ampere produced by the source.

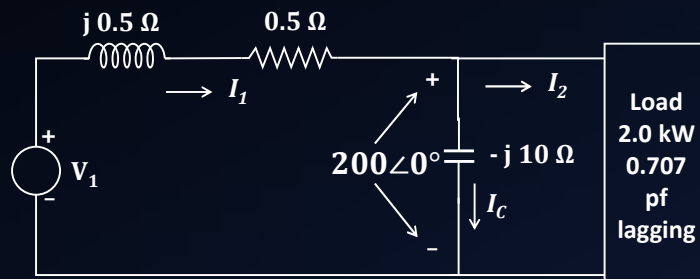



Example 3

Solution

$$P = VI \cos \theta$$

$$\therefore I_2 = \frac{2.0 \times 10^3}{200 \times 0.707} = 14.14 \text{ A}$$

$$\begin{aligned} I_2 &= 14.14 (\cos \theta - \sin \theta) \\ &= 14.14 (0.707 + \sin [\cos^{-1} 0.707]) \\ &= 10 - j10 \end{aligned}$$

The current through the capacitor.

$$I_c = \frac{200 \angle 0^\circ}{10 \angle -90^\circ} = 20 \angle 90^\circ = j20$$



Example 3

Solution (Contd...)

The supply current

$$I_1 = I_2 + I_c = 10 - j10 + j20 = 10 + j10 = 14.14 \angle 45^\circ$$

The source voltage

$$\begin{aligned} V_1 &= 200 + (10 + j10)(0.5 + j0.5) \\ &= 200 + j10 = 200.25 \angle 2.86^\circ \text{ V} \end{aligned}$$

The volt-ampere

$$VA = 200.25 \times 14.14 = 2831.535 \text{ VA}$$



Example 3

Solution (Contd...)

The power factor angle

$$\theta = 2.86^\circ - 45^\circ = -42.14^\circ$$

The power

$$P = 200.25 \times 14.14 \cos(-42.14^\circ) = 2099.6W$$


Reactive power

$$Q = 200.25 \times 14.14 \sin(-42.14^\circ) = -1899.9 VAR$$
$$= 1899.9 VAR \text{ (capacitive)}$$



Example 4

For the distribution system shown in Fig., a load of 10 kW at power factor 0.8 lagging is supplied to two sources of voltages V_1 and V_2 . The source V_2 supplies 5 kW at 0.6 power factor lagging. Find (a) the two-source voltages V_1 and V_2 and (b) the volt-ampere and power factor of the source V_1 .

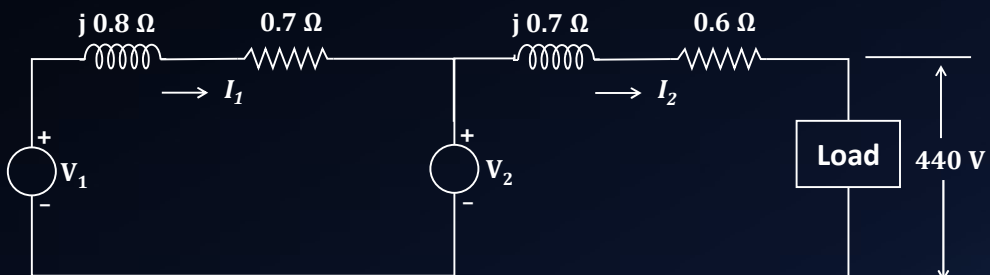



Example 4

Solution

The load current

$$I_L = \frac{10 \times 100}{440 \times 0.8} = 28.41 \text{ A}$$

In complex form,

$$I_L = 28.41 \times 0.8 - j28.41 \times 0.6 = 22.73 - j17.05$$

Reactive power of the load

$$Q_L = \frac{P_L}{0.8} \times 0.6 = \frac{10}{0.8} \times 0.6 = 7.5 \text{ kVAR}$$



Example 4

Solution (Contd...)

The voltage $V_2 = 440 + j0 + (22.73 - j17.05)(0.6 + j0.7)$

$$= 465.57 + j5.68 = 465.6 \angle 0.7^\circ$$

The current supplied by V_2 ,

$$I_2 = \frac{5 \times 1000}{465.6 \times 0.6} = 17.9 \text{ A}$$

The power factor angle of V_2 ,

$$\theta_2 = \cos^{-1} 0.6 = 53.13^\circ$$

So, the phasor angle of I_2 ,

$$\theta_2 = -(53.13 - 0.7) = -52.43^\circ$$

$$I_2 = 17.9 \cos(-52.43^\circ) + j17.9 \sin(-52.43^\circ)$$

$$I_2 = 10.9 - j14.19$$

Hence, $I_1 = I_L - I_2 = 22.73 - j17.05 - 10.9 + j14.19$

$$I_1 = 11.83 - j2.86 = 12.17 \angle -13.6^\circ$$



Example 4

Solution (Contd...)

The total power and reactive power supplied by the two sources are given by

$$P = P_L + I_L^2 \times 0.6 + I_1^2 \times 0.7 = 10.588 \text{ kW}$$

$$Q = 7.5 + [28.41^2 \times 0.7 + 12.7^2 \times 0.8] \times 10^{-3} = 8.183 \text{ kVAR}$$

Voltage of the source V_1 ,

$$V_1 = V_2 + I_1 \times (0.7 + j0.8) = 476.32 \angle 1.58^\circ$$

The power, reactive power and KVA supplied by source



Example 4

Solution (Contd...)

The power, reactive power and KVA supplied by source

$$P_{r_1} = P - P_{r_2} = 10.588 - 5 = 5.588 \text{ kW}$$

$$Q_{r_1} = Q - Q_{r_2}$$

$$Q_{r_2} = \frac{5}{0.6} \sin(\cos^{-1} 0.6) = \frac{5 \times 0.8}{0.6} = 6.66$$

$$\therefore Q_{r_1} = 8.183 - 6.66 = 1.52 \text{ kVAR}$$

$$\text{kVA} = \sqrt{5.588^2 + 1.52^2} = 5.79 \text{ kVA}$$

$$\text{Power Factor} = \cos(\tan^{-1} \frac{1.52}{5.88}) = 0.965 \text{ lagging}$$



Example 5

Find the resonance frequency for a series circuit, if $L = 32 \mu H$ and $C = 450 pF$. Determine required value of R for the quality factor $Q = 0.05$. Find lower and upper cut off frequencies and bandwidth.

Solution

The resonance frequency, $f_r = \frac{1}{2\pi\sqrt{LC}} = 1.33 \text{ MHz}$

The quality factor, $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

$$\therefore R = \sqrt{\frac{L}{CQ^2}} = 5.33 \text{ k}\Omega$$



Example 5

Solution (Contd...)

The lower cut off frequency, $f_1 = -\frac{f_r}{2Q} + f_r \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} = 66.33 \text{ kHz}$

The upper cut off frequency, $f_2 = \frac{f_r}{2Q} + f_r \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} = 26670 \text{ kHz}$

Bandwidth = $f_2 - f_1 = 26603.67 \text{ kHz}$



Example 6

An inductive coil having resistance of $20\ \Omega$ and inductance of $0.2\ H$ is connected in parallel with a $100\ \mu F$ capacitor. Calculate the frequency at which the circuit acts as a non-reactive resistor R . Find the value of R

Solution

The admittance of the parallel circuit, $Y = \frac{1}{R+j\omega L} + j\omega C = \frac{R-j\omega(L-\omega^2 CL^2-CR^2)}{R^2 + \omega^2 L^2}$

For the circuit to be non inductive, $L - \omega^2 CL^2 - CR^2 = 0$

Accordingly, $\omega = \sqrt{\frac{1}{CL} - \frac{R^2}{L^2}} = 200$

Hence $f_r = \frac{200}{2\pi} = 31.8\ Hz$



Example 6

Solution (Contd...)

$$\therefore Y = \frac{R}{R^2 + \omega^2 L^2} \Rightarrow Z = \frac{1}{Y} = R'$$

The non reactive resistance, $R' = \frac{R^2 + \omega^2 L^2}{R} = 100\ \Omega$