



Basic Electrical Engg – EE102 (Lecture Notes – 3 Phase AC Circuits) (PART-1)

Topics Covered

- ✓ 3 Phase EMF Generation
- ✓ Delta and Star Connection
- ✓ Line and Phase Quantities
- ✗ Solution of 3 Phase Circuits
- ✓ Balanced Supply and Balanced Load
- ✓ Phasor Diagram
- ✗ 3 Phase Power Measurement by 2-Wattmeter Method



Three Phase Emf Generation - Three phase circuits

Synchronous generator - (Alternators)

Three phase power


Single phase power

- Stator
 - Stator frame
 - Stator core
 - Stator winding


Star connected Delta connected

- Rotor
 - Salient pole type (low speed)
 - Cylindrical type (High speed)
- Rotor core
- Rotor windings

- slip rings, brushes
- Air gap.

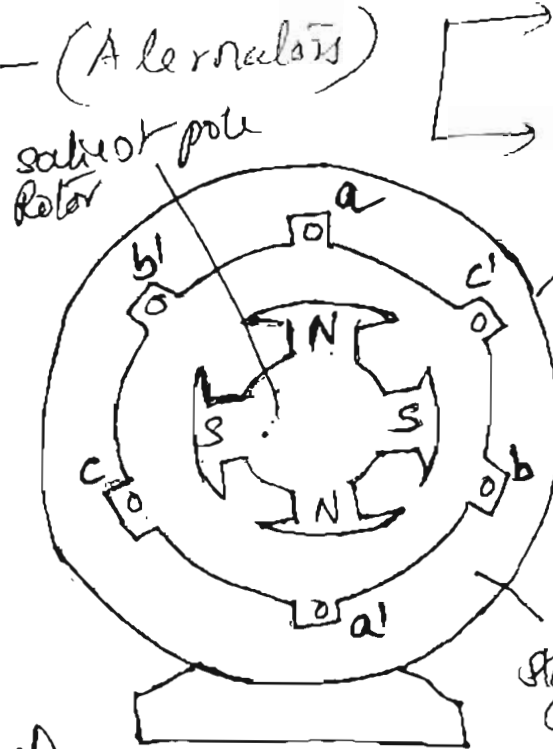

Salient pole syn. generator

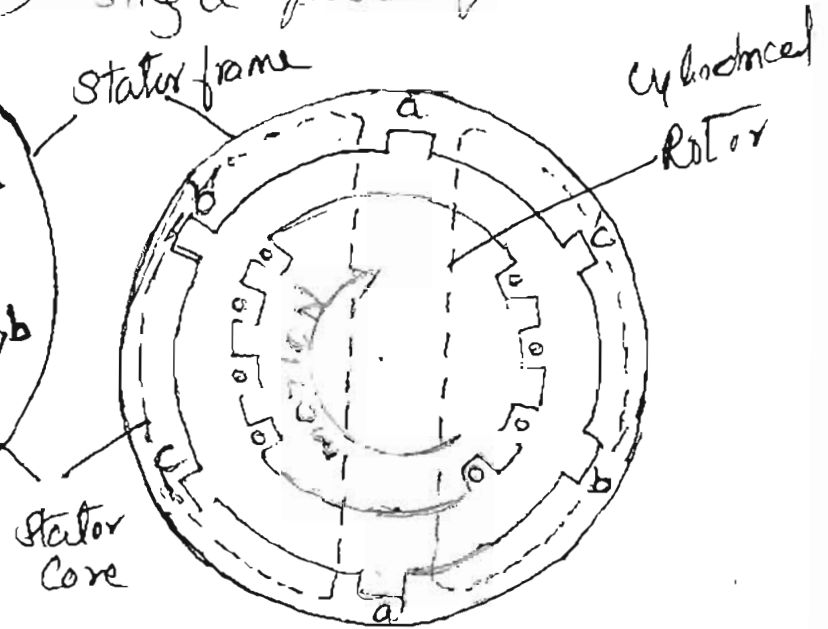

Cylindrical rotor syn. generator.


Rotor \rightarrow Prime mover \rightarrow Water turbine - low speed
 \downarrow \rightarrow Steam turbine \rightarrow high speed

At fixed speed $N_s \rightarrow$ synchronous speed.

Rotor windings \rightarrow dc excitation \rightarrow field \rightarrow Airgap.

When rotor is stand still with field excitation \rightarrow no emf in the stator windings

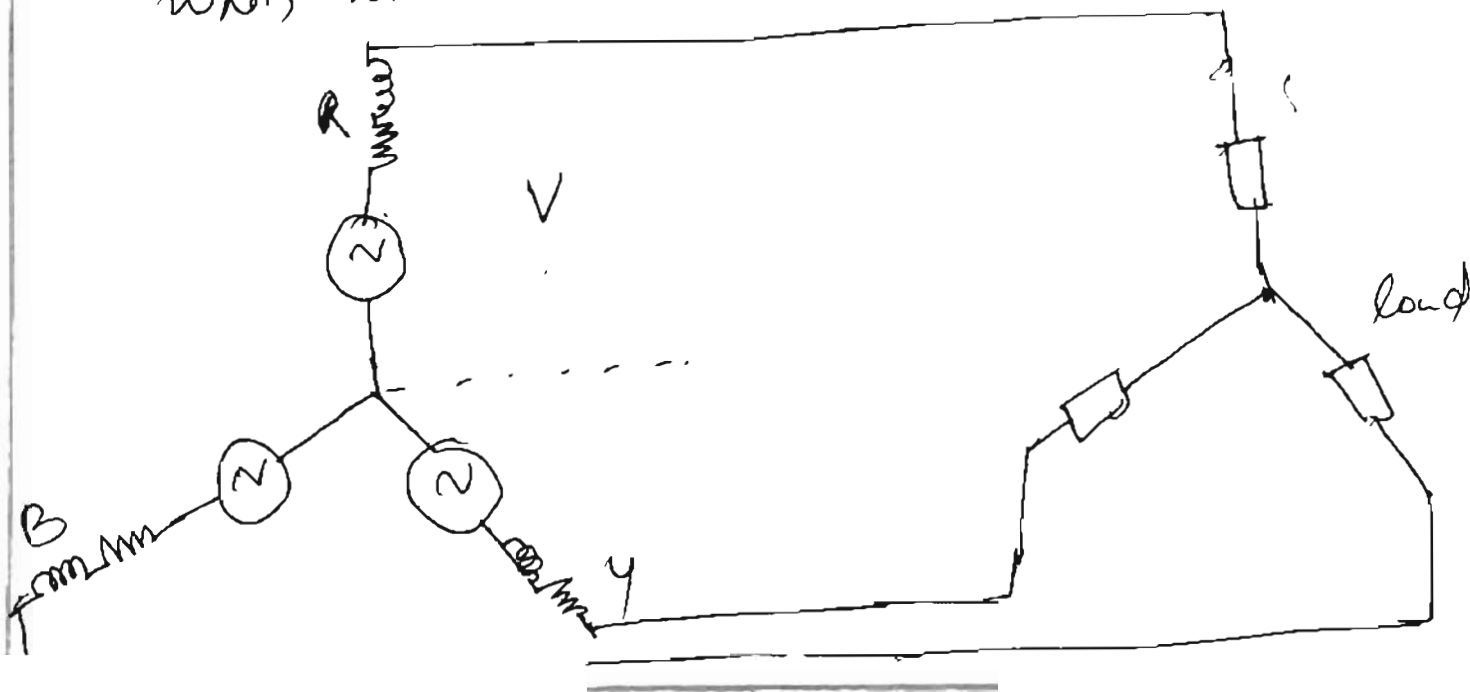
When rotor is driving and field excitation on \rightarrow emf is induced in the stator windings



3


In a 3 phase system, three voltages are generated by the 3 phase windings of a three phase syn. generator. The three windings may be connected in star or delta.

Star

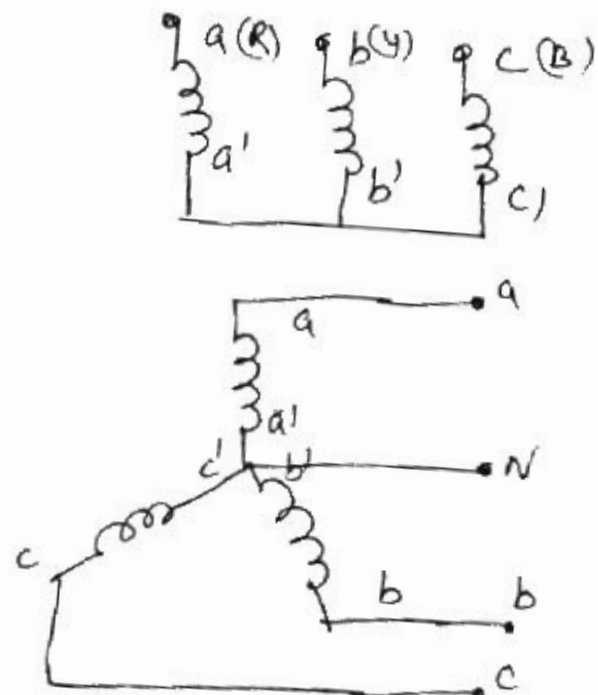


3 wire system / 4 wire wire (Neutral)

Delta

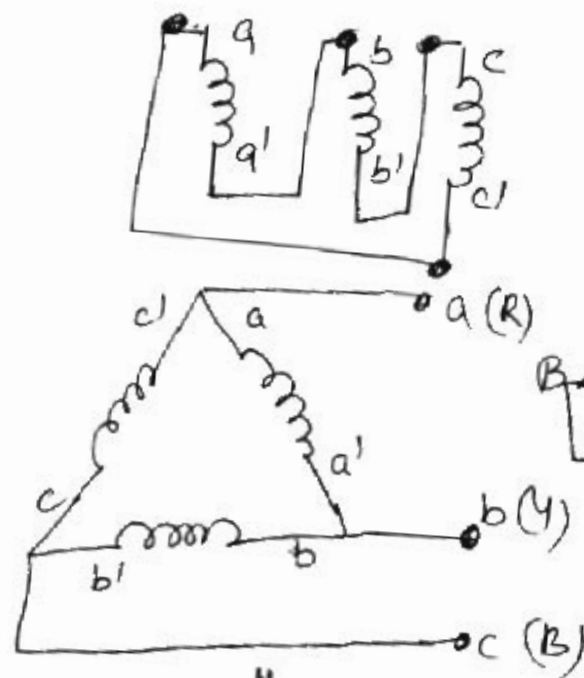

Three wire system

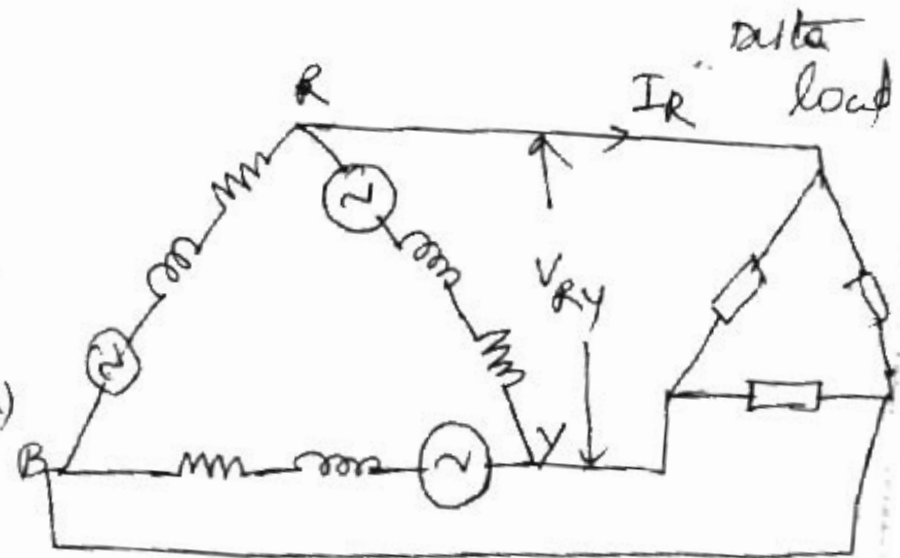

Advantages of Three phase system

- Three phase Transmission line cheaper \rightarrow same P, V.
- \rightarrow Three phase IM \rightarrow more efficient.
- \rightarrow " " better pf than 1 phase
- \rightarrow " " provides uniform torque IM.
- \rightarrow Three phase IM \rightarrow self starting
- 1 phase IM \rightarrow Auxiliary winding for starting
- \rightarrow Three phase system has better Voltage Regulation.
- \rightarrow For a given size and frame, the Power generated by a 3 Phase alternator is high

PS \rightarrow Generation, Transmission, Distribution


(a) \downarrow 11 kV/33

(b) 400 kV/765 kV


(c) 33 kV/11 kV

(d) Utilization \rightarrow Three phase (400V, 50 Hz)
 \rightarrow Single phase (230V, 50 Hz)

Three Phase Voltages, currents and Power

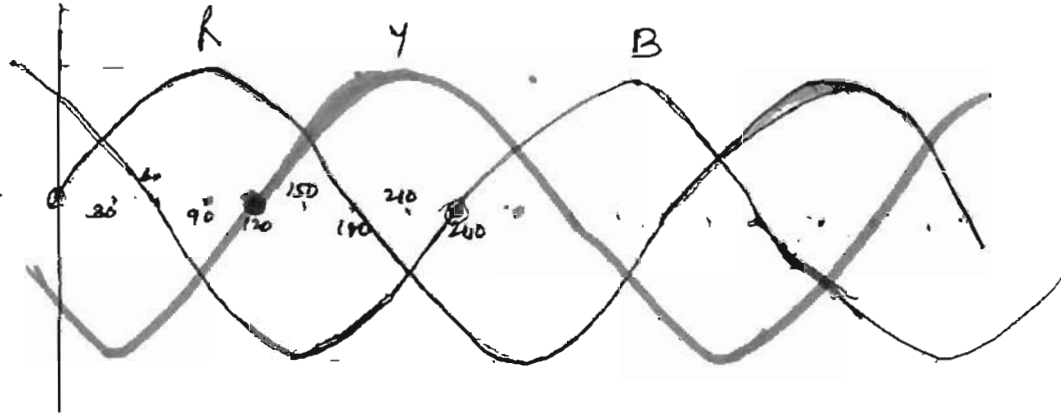


Balanced system

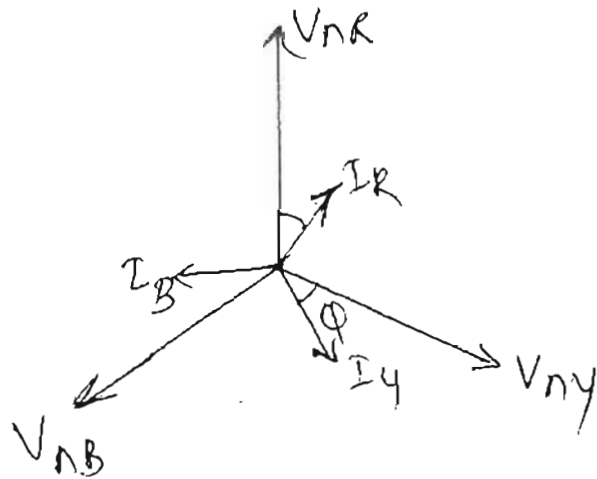

When loads connected to the three phase are equal the currents in the three phases are equal in magnitude and displaced in phase by 120° .

Unbalanced system

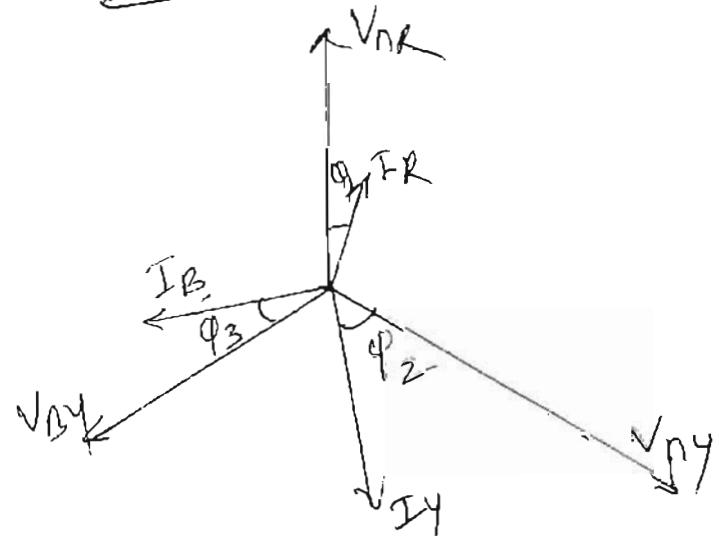

Balanced system

$$V_{nR} = V_{L0} = V_m \sin \omega t$$

$$V_{ny} = V \angle -120^\circ = V_m \sin(\omega t - 120^\circ)$$


$$V_{nB} = V \angle -240^\circ = V_m \sin(\omega t - 240^\circ) = V_m \sin(\omega t + 120^\circ)$$

Power

$P \rightarrow$ 3 phase load \rightarrow sum of P of each phase.

$$P = 3 V_p I_p \cos \phi$$

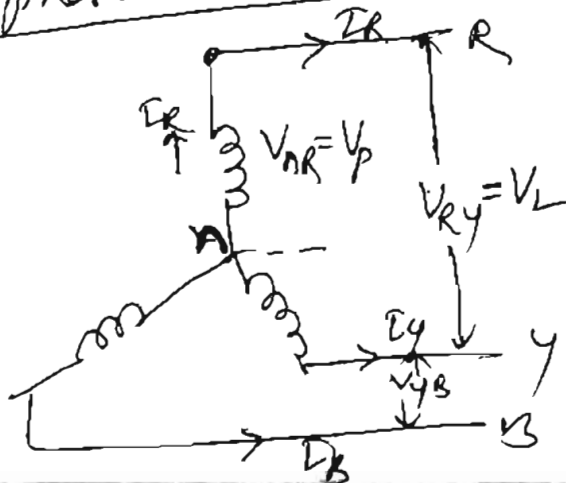Line and phase voltages and currents in
3 phase star connection




$$V_p = V_{nR} = V_{ny} = V_{nB}$$

$$V_L = V_{RY} = V_{YB} = V_{BR}$$

$$I_R = I_Y = I_B = I_p = I_L$$

KVL \rightarrow RnY
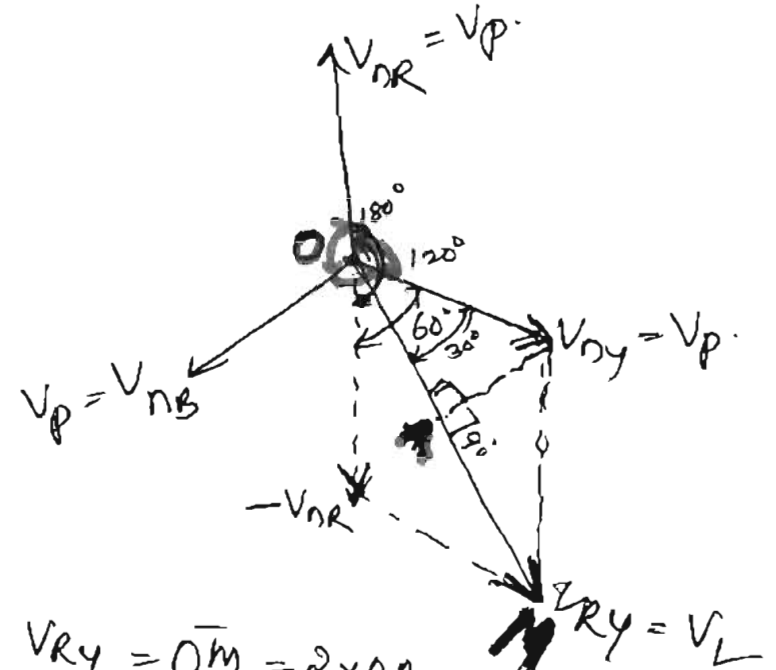
$$V_{RY} = V_{nR} + V_{ny} = -V_{nR} + V_{ny}$$



$$V_{RY} = 0^\circ = 2 \times 0^\circ$$

$$V_L = 2 \times V_{ny} \cos 30^\circ = 2 \times V_p \times \frac{\sqrt{3}}{2}$$

$$V_L = \sqrt{3} V_p$$

$$I_L = I_p$$

OR

$$V_{RY} = V_L = -V_{NR} + V_{NY}$$

$$= -V_p \angle 0^\circ + V_p \angle 120^\circ$$

$$= -V_p + V_p (\cos 120^\circ - j \sin 120^\circ)$$

$$= -V_p + V_p \left(-\frac{1}{2} - j \frac{\sqrt{3}}{2}\right)$$

$$= V_p \left(-\frac{3}{2} - j \frac{\sqrt{3}}{2}\right)$$

$$= \sqrt{3} V_p \left(-\frac{\sqrt{3}}{2} - j \frac{1}{2}\right)$$

$$\underline{V_L = \sqrt{3} V_p \angle -150^\circ}$$



As $\angle -150^\circ = \cos(-150^\circ) + j \sin(-150^\circ)$

$$\boxed{V_L = \sqrt{3} V_p}$$

$$I_L = I_p$$

Star

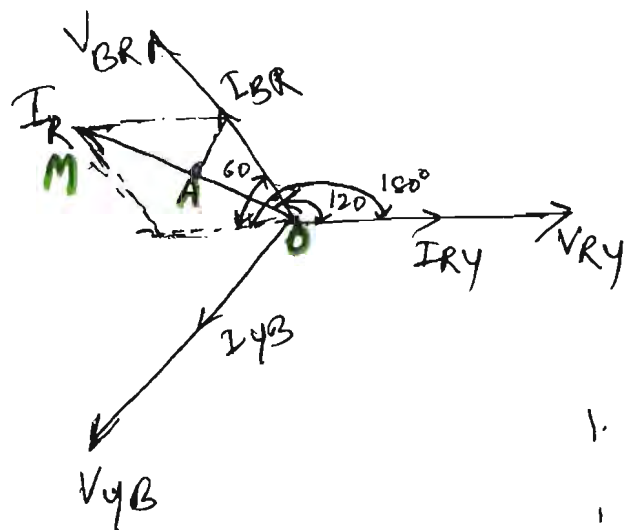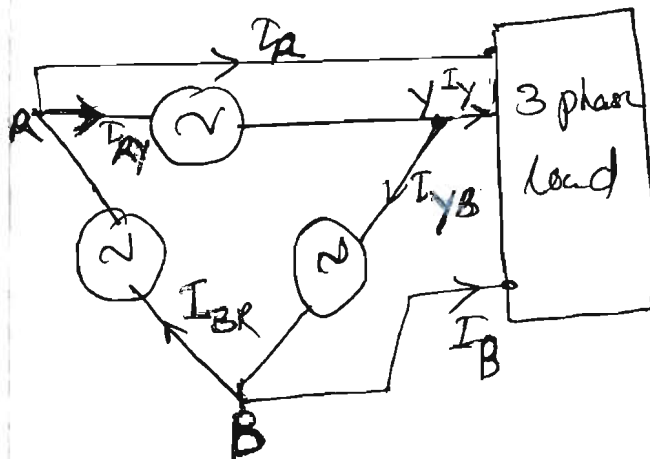Line and phase voltages and currents in 3 phase delta connection



KCL at node R

$$I_R = I_{BR} - I_{RY}$$

$$I_{RY} = I_p \angle 0^\circ$$

$$I_{YB} = I_p \angle -120^\circ$$

$$I_{BR} = I_p \angle 120^\circ$$

$$I_R = I_{BR} - I_{RY} = I_p \angle 120^\circ - I_p \angle 0^\circ$$

$$= I_p \left(-\frac{3}{2} + j \frac{\sqrt{3}}{2}\right) = \sqrt{3} I_p \angle 150^\circ$$

$$\therefore \boxed{V_L = V_p}$$

$$\boxed{I_L = \sqrt{3} I_p}$$

Delta



$$1. \therefore I_R = OM = 2 \times OA$$

$$= 2 \times I_{BR} \cos 30^\circ$$

$$I_R = I_L = 2 \times I_p \frac{\sqrt{3}}{2}$$

$$= \underline{\underline{\sqrt{3} I_p}}$$

Balanced Three phase star connected load

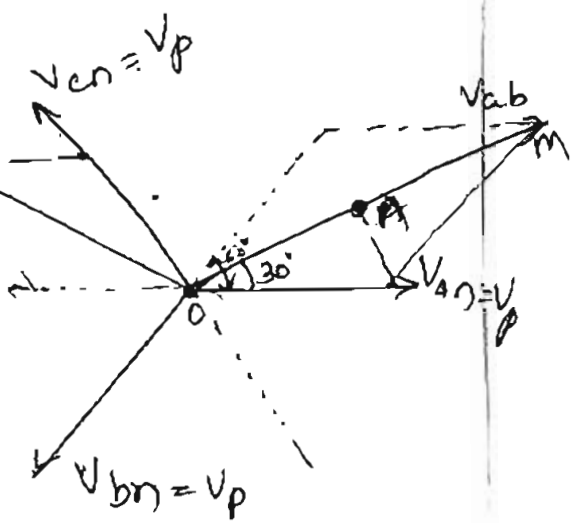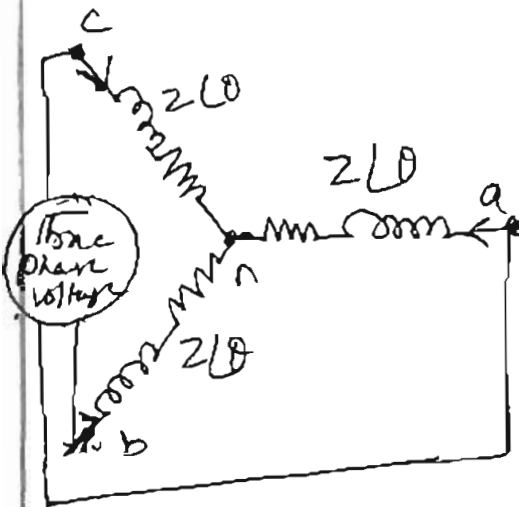

$$V_{ab} = V_L = V_{an} + V_{nb} = \overline{OM} = 2 \times OA = 2 \times V_{an} \cos 30^\circ$$

$$V_L = \sqrt{3} V_p$$

OR $V_{ab} = V_p \angle 0^\circ - V_p \angle -120^\circ$
 $= V_p - V_p \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right)$
 $= V_p \left(\frac{3}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \left[\frac{\sqrt{3}}{2} + j\frac{1}{2} \right]$


$$V_{ab} = V_L = \sqrt{3} V_p \angle 30^\circ$$

V_L leads V_p by 30°

$$V_L = \sqrt{3} V_p$$

$$I_L = I_p$$

Balanced Delta connected load

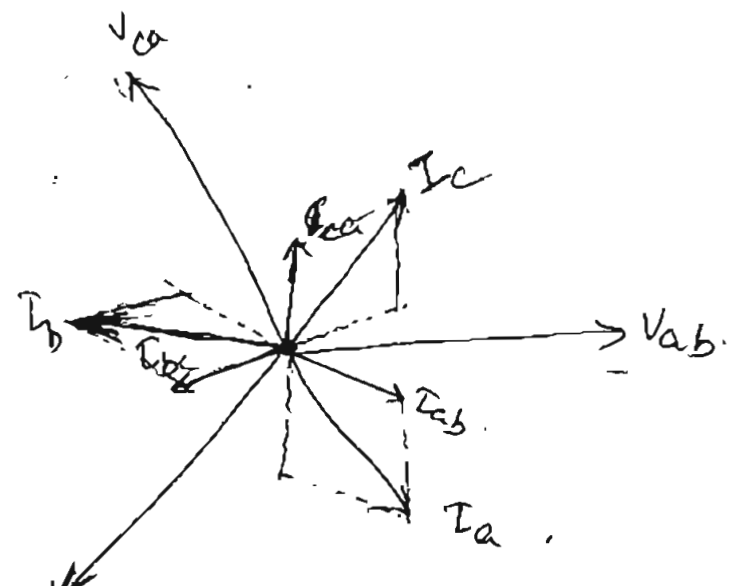

KLC nodal V_{bc}

$$I_a = I_{ab} - I_{ca}$$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

Delta connected load (Continued)

$$I_{ab} = \frac{V_{ab}}{Z_{\Delta}} = \frac{V_L \angle 0}{Z_{\Delta}} = \frac{V_L \angle 0}{Z}$$

$$I_{bc} = \frac{V_{bc}}{Z_{\Delta}} = \frac{V_L \angle -120}{Z_{\Delta}} = \frac{V_L \angle -(120 + \theta)}{Z}$$

$$I_{ca} = \frac{V_{ca}}{Z_{\Delta}} = \frac{V_L \angle 120}{Z_{\Delta}} = \frac{V_L \angle (120 - \theta)}{Z}$$

Star connected load

$$I_a = \frac{V_{an}}{Z_{\Delta}} = \frac{V_p \angle 0}{Z_{\Delta}} = \frac{V_p \angle 0}{Z}$$

$$I_b = \frac{V_{bn}}{Z_{\Delta}} = \frac{V_p \angle -120}{Z_{\Delta}} = \frac{V_p \angle -(120 + \theta)}{Z}$$

$$I_c = \frac{V_{cn}}{Z_{\Delta}} = \frac{V_p \angle 120}{Z_{\Delta}} = \frac{V_p \angle 120 - \theta}{Z}$$

Power in Three Phase Balanced system

Active Power in each phase $P_a = P_b = P_c = V_p I_p \cos \theta$

Total power $P = P_a + P_b + P_c = \underline{3 V_p I_p \cos \theta}$

For star connection

$$V_L = \sqrt{3} V_p ; I_L = I_p$$

$$\therefore P = \boxed{3 V_p I_p \cos \theta}$$

$$P = 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta = \boxed{\sqrt{3} V_L I_L \cos \theta}$$

For Delta connection

$$P = \boxed{3 V_p I_p \cos \theta}$$

$$P = 3 V_L \frac{I_L}{\sqrt{3}} \cos \theta$$

$$= \boxed{\sqrt{3} V_L I_L \cos \theta}$$

$$\begin{aligned} V_L &= V_p \\ I_L &= \sqrt{3} I_p \end{aligned}$$

Active, Reactive and Apparent Power

$$P = 3V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$\text{Apparent Power } S = 3V_p I_p = \sqrt{3} V_L I_L$$

$$\text{Reactive Power } Q = 3V_p I_p \sin \theta = \sqrt{3} V_L I_L \sin \theta$$

Phase sequence

ABC (R Y B) \rightarrow B' phase voltage lags A' phase voltage by 120° and C' phase voltage lags A' phase voltage by 240° .

in ACB (R B Y) \rightarrow C' ~~lags~~ lags A' by 120° & 240° respectively.

Reversal of phase sequence \rightarrow reverses the direction of rotation of motor