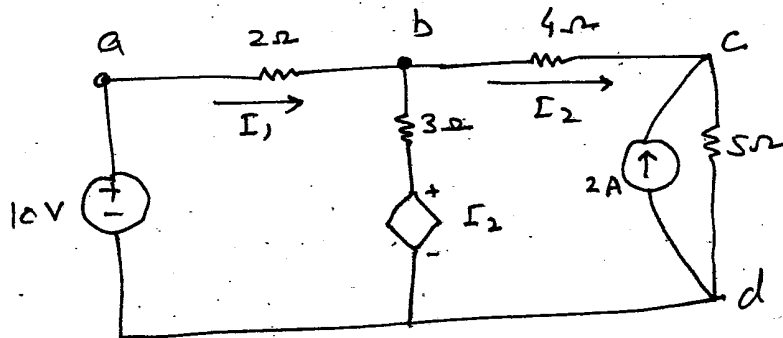


UNIT 11 Supple

Dependant Sources



Q1 9/Assign 2.

- (a) Find value of I_1
 (b) Thevenin's Equivalent between c and d removing current source of 2A and 5Ω resistance.




Soln:

For Voc

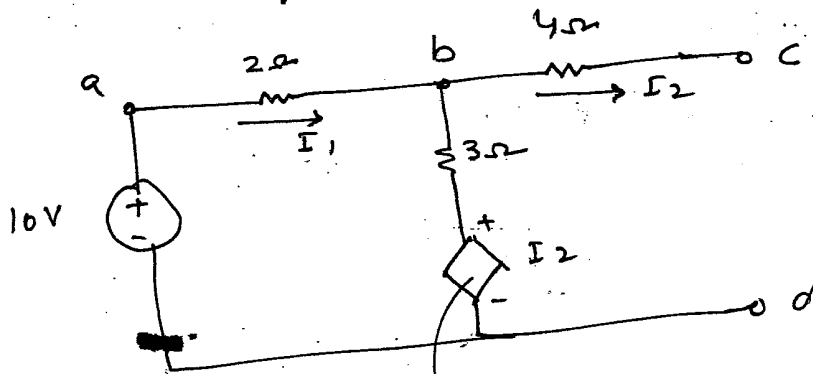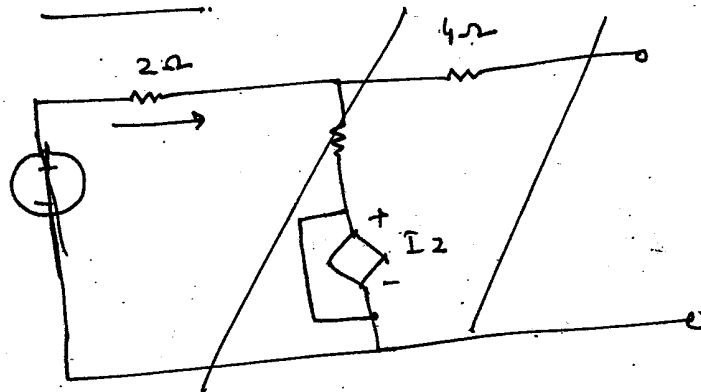


$I_2 = 0$; so This is 0 i.e. SC

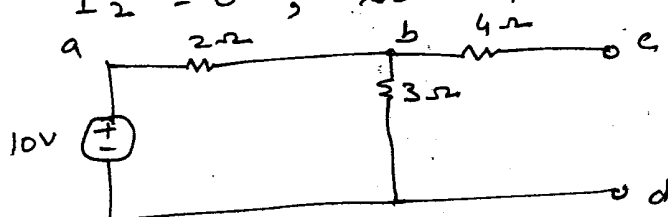

$$V_{td} = V_{bd} = \frac{3 \times 10}{5} = 6V$$

To find I_{sc}

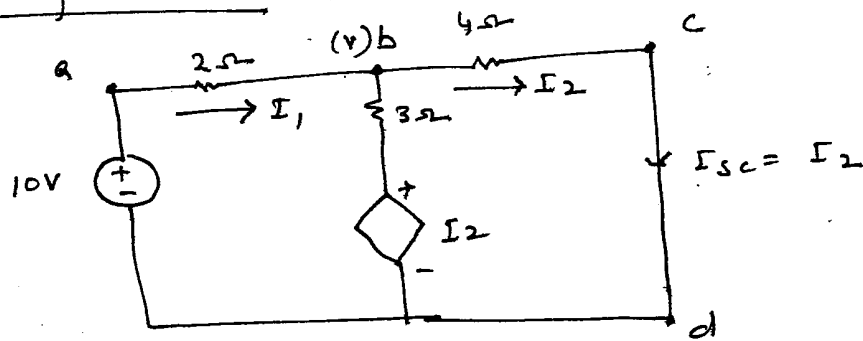

$$\frac{10 - V}{2} - \frac{V}{4} - \frac{V - I_2}{3} = 0$$

(I₁) (I₂)

$$\frac{10 - V}{2} - \frac{V}{4} - \frac{V - (\frac{V}{4})}{3} = 0$$

$$5 - \frac{V}{2} - \frac{V}{4} - \frac{3V}{12} = 0$$

$$5 - \frac{V}{2} - \frac{V}{4} - \frac{V}{4} = 0$$


$$5 - V = 0$$

$$V = 5$$

$$I_2 = I_{sc} = \frac{5}{4} \text{ A}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{6}{5/4} = \frac{24}{5} \Omega \text{ Ans.}$$

To find R_{Th}

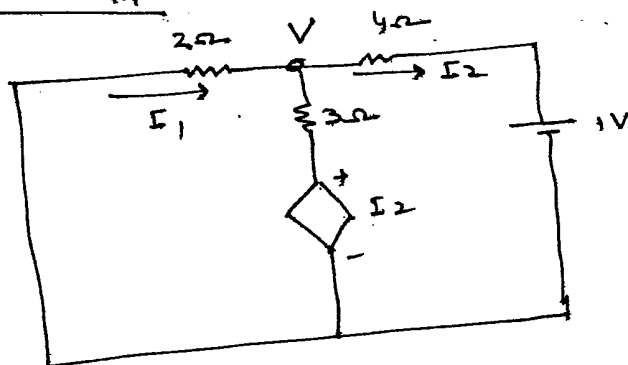

$$-\frac{V}{2} - \frac{V - I_2}{3} - \frac{V - 1}{4} = 0$$

$$-\frac{V}{2} - \frac{V - (\frac{V-1}{4})}{3} - \frac{V-1}{4} = 0$$

$$-\frac{V}{2} - \frac{4V - V + 1}{3 \cdot 4} - \frac{V-1}{4} = 0$$

$$\frac{V}{2} - \frac{3V+1}{12} - \frac{V-1}{4} = 0$$

$$-\frac{V}{2} - \frac{V}{4} - \frac{1}{12} - \frac{V}{4} + \frac{1}{4} = 0$$

$$-V - \frac{1}{12} + \frac{1}{4} = 0$$

$$-V + \frac{2}{12} = 0$$

$$-V + \frac{1}{6} = 0$$


$$V = +\frac{1}{6}$$

$$V = 6V$$

$$I_2 = \frac{6-1}{4} = \frac{5}{4} = 1.25 \quad -\frac{5/6}{4} = -\frac{5}{24}$$

$$R_{Th} = \frac{1}{\frac{1}{4} + \frac{5}{24}} = \frac{1}{\frac{8+5}{24}} = \frac{24}{13} \Omega$$

Q2 Determine R_{Th} at a, b

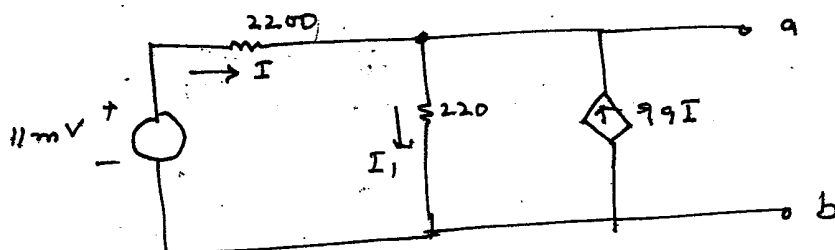

KCL at a

$$-I + I_1 - 99I = 0$$

$$I_1 = 100I$$

KVL for Left loop


$$-11 \times 10^{-3} + 2200I + 220I_1 = 0$$

$$I_1 = 45.5 \mu A$$

$$V_{oc} = 220 \cdot I_1 = 10 mV$$

$$\begin{cases} -11 \times 10^{-3} + 2200I + 22000I = 0 \\ -11 \times 10^{-3} + 22I_1 + 220I_1 = 0 \\ 242I_1 = 11 \times 10^{-3} \\ I_1 = \frac{11 \times 10^{-3}}{242} = \frac{1 \times 10^{-3}}{22} = \frac{1000 \times 10^{-6}}{22} = 45.5 \mu A \end{cases}$$

For SC

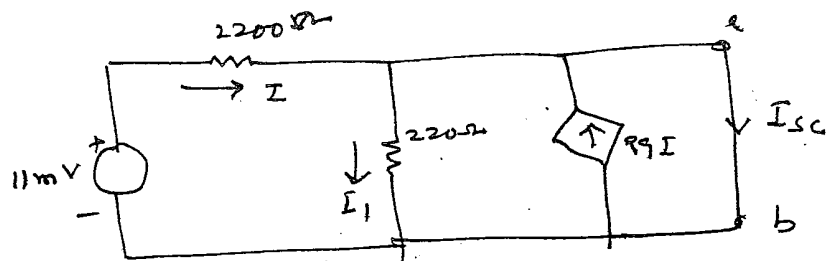

$$V_{ab} = 0 \quad I_1 = 0$$

KCL gives

$$-I - 99I + I_{sc} = 0 \quad I_{sc} = 100I$$

KVL on outer loop.


$$-11 \times 10^{-3} + I \times 2200 = 0$$

$$I = 5 \mu A$$

$$I_{sc} = 100I = 500 \mu A$$

$$R_{Th} = \frac{V_{oc}}{I_s} = \frac{10 \times 10^{-3}}{500 \times 10^{-6}} = 20 \Omega \quad \text{Ans.}$$

Alternatively

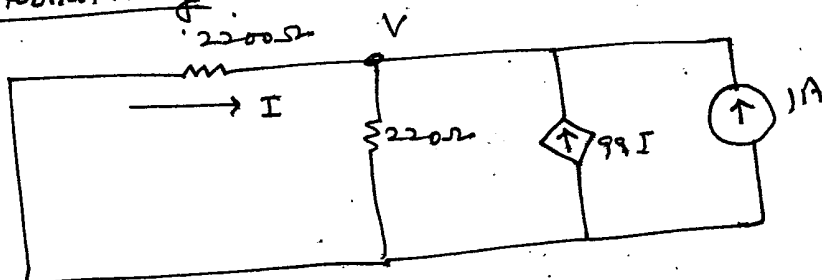

$$\frac{V}{2200} + \frac{V}{220} - 99I - 1 = 0$$

$$\left[I = \frac{-V}{2200} \right]$$

$$\frac{V}{2200} + \frac{V}{220} + 99 \frac{V}{2200} = 1$$

$$\frac{100V}{2200} + \frac{V}{220} = 1$$

$$\frac{V}{22} + \frac{V}{220} = 1$$

$$\frac{V}{220} [10 + 1] = 1$$


$$\frac{11V}{220} = 1 \quad \therefore \frac{V}{20} = 1 \quad \therefore V = 20 \text{ volts}$$

$$R_{Th} = \frac{20}{1} = 20 \Omega \quad \text{Ans.}$$


★

①

$$M = M_{12}(+)$$

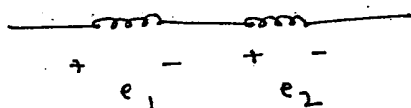

$e_1 + e_2$ = induced voltage

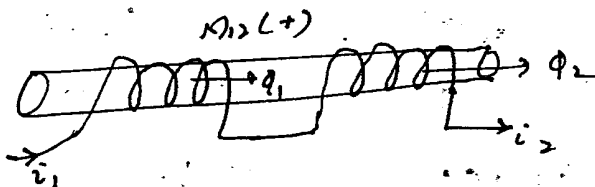

Φ_1 & Φ_2 are in the same direction

$$e_1 = L_1 \frac{di_1}{dt} + M_{12} \frac{di_2}{dt}$$

if $i_1 = i_2 = i$

$$e_1 = L_1 \frac{di}{dt} + M_{12} \frac{di}{dt}$$

$$= (L_1 + M_{12}) \frac{di}{dt}$$

Also $e_2 = (L_2 + M_{12}) \frac{di}{dt}$


$$e_T = e_1 + e_2 = (L_1 + M_{12}) \frac{di}{dt} + (L_2 + M_{12}) \frac{di}{dt}$$

$$= (L_1 + L_2 + M_{12} + M_{12}) \frac{di}{dt}$$

$$L_T(+) = L_1 + L_2 + 2 M_{12}$$

①

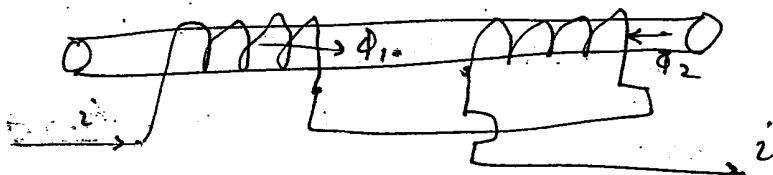But if coils are connected in the opposite direction



Φ_1 & Φ_2 are in opposite direction

$$L_T(-) = L_1 + L_2 - 2 M_{12}$$

②

From eqs ① and ②

$$M = \frac{1}{4} [L_T(+) - L_T(-)] \quad \text{--- 3}$$

$$Q = 10 \sin \omega t - 17.3 \cos \omega t$$

$$= 20 \left[\frac{1}{2} \sin \omega t - \frac{\sqrt{3}}{2} \cos \omega t \right]$$

$$= 20 \left[\cos 60^\circ \sin \omega t - \sin 60^\circ \cos \omega t \right]$$

$$= 20 \left[\sin (\omega t - 60^\circ) \right] \quad \text{why not } \frac{\pi}{3}?$$

$$Q_m = \underline{20}$$

$$Q_{rms} = \frac{20}{\sqrt{2}} = \underline{14.14} \quad \text{Discuss}$$

Example 4: An emf is given by $e = 170 \sin 314 t$

Determine

- (i) maximum value
- (ii) rms value
- (iii) frequency
- (iv) radians through which its vector has gone when $t = 0.001$ sec and
- (v) value of e at the above instant

Soln:

$$(i) E_m = \underline{170} \quad (ii) E_{rms} = \frac{170}{\sqrt{2}} = \underline{120.23 V}$$

$$(iii) f = \frac{\omega}{2\pi} = \frac{314}{2 \times 3.14} = \underline{50 \text{ Hz (C/s)}}$$

$$(iv) \omega t = 2\pi f t = 2 \cdot \pi \cdot 50 \cdot 0.001 \\ = \underline{0.314 \text{ radians}}$$

$$(v) e = 170 \sin 314 t \\ = 170 \sin 314 \times 0.001 \\ = 170 \sin (0.314) \\ = 170 \sin \left(\frac{314 \times 180}{\pi} \right)^\circ \\ = 170 \sin 18^\circ = 170 \times 0.31 = \underline{52.7 V}$$

Example 5: If ~~$v = 141.42 \sin(157.08t + \pi/2)$~~

~~Find~~ If $i = 10 + 10 \sin 314t$

& Find I_{rms} & I_{av}

Soln


$$I_{rms} = \sqrt{10^2 + \left(\frac{10}{\sqrt{2}}\right)^2} = \sqrt{100 + 50}$$

$$= \sqrt{150} = 12.25 \text{ A}$$

$$I_{av} : 10 \text{ A}$$

As average value of $10 \sin 314t$ over the complete cycle is zero.

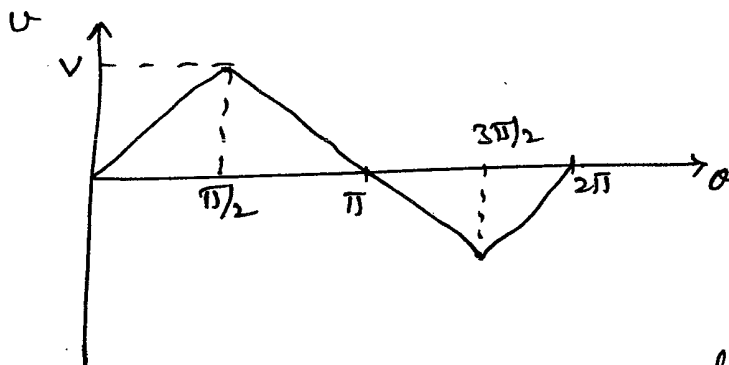Example 6: Determine the rms and average value of the wave form shown:



Soln.

$$V_{av} = \frac{\text{Area under the curve for 1 quarter}}{\text{base}}$$

$$= \frac{\frac{1}{2} V_m \cdot \pi/2}{\pi/2} = 0.5 V_m$$

$V_{rms} :$ (Consider only 1 quarter)

$$v = m\alpha$$

$$m \text{ is slope} = \frac{2V_m}{\pi}$$

Mean square value: $\therefore v = \frac{2V_m}{\pi} \alpha$
 $\frac{\text{Area under squared wave}}{\text{base}}$

$$= \frac{2}{\pi} \int_0^{\pi/2} v^2 d\alpha = \frac{2}{\pi} \int_0^{\pi/2} \left(\frac{2V_m}{\pi} \alpha\right)^2 d\alpha = \frac{2}{\pi} \cdot \frac{4V_m^2}{\pi^2} \cdot \frac{\pi^3}{24} = \frac{2}{3} V_m^2$$

$$\begin{aligned}
&= \frac{2}{\pi} \int_0^{\pi/2} \frac{4V_m^2 \theta^2}{\pi^2} d\theta \\
&= \frac{2}{\pi} \cdot \frac{4V_m^2}{\pi^2} \int_0^{\pi/2} \theta^2 d\theta \\
&= \frac{8V_m^2}{\pi^3} \left[\frac{\theta^3}{3} \right]_0^{\pi/2} \\
&= \frac{8V_m^2}{\pi^3 \cdot 3} \left[\theta^3 \right]_0^{\pi/2} \\
&= \frac{8V_m^2}{3\pi^3} \left[\frac{\pi^3}{8} - 0 \right] \\
&= \frac{8V_m^2}{3\pi^3} \cdot \frac{\pi^3}{8} = \frac{V_m^2}{3}
\end{aligned}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{3}} = \frac{V_m}{\sqrt{3}} = \underline{0.577 V_m}$$

Example: 7

$$i_1 = 100 \sin(\text{~~100t~~})$$

$$= 100 \sin(314t)$$

$$i_2 = 100 \sin(314t - 60^\circ)$$

(i) Draw these wave forms on a graph paper to the scale

(ii) Add them

(iii) Write down the expression for $(i_1 + i_2)$

Soln: Graphically - - - do as an assignment

Analytically

$$i_1 + i_2 = 100 \sin(314t) + 100 \sin(314t - 60^\circ)$$

$$= \underline{100 \left[\frac{1}{2} \sin 314t + \frac{1}{2} \sin \right]}$$

$$\begin{aligned}
 i_1 + i_2 &= 100 \sin 314t + 100 \sin (314t - 60^\circ) \\
 &= 100 \left[2 \cdot \sin (314t - 30^\circ) \cos 30^\circ \right] \\
 &= 100 \left[\frac{2\sqrt{3}}{2} \sin (314t - 30^\circ) \right] \\
 &= 100 \left[1.732 \sin (314t - 30^\circ) \right] \\
 &= 173.2 \sin (314t - 30^\circ)
 \end{aligned}$$

Comment: So $(i_1 + i_2)$ is also a sinusoid with a phase angle changed.

Example: 8 $i_1 = 100 \sin 314t$
 $i_2 = 100 \sin 628t$

Repeat the example 7.

Soln: The result wouldn't be a pure sinusoid

Therefore, sinusoidal
 the quantities with different frequencies
 when added do not give pure sinusoid.
 So, it would be difficult to perform
 algebraic operations for them.